

## Simple SWL HF- VHF Receiver

From the book *“DX Reception”* (by Igor Grigorov (RK3ZK), Belgorod, 1994), pp.:76- 81.  
(Article published with inessential cutting)  
See ANTENTOP- 01- 2007, p.p.: 73- 74.

Using only 4 cheap surplus transistors and 1 mixer SBL- 1 you can do a HF- VHF receiver that provides good reception on HF (12- 29- MHz) and ex- Soviet BC FM VHF- 61- 88 MHz. Receiver catches AM and FM with deviation more the 25 kHz. Such receiver allows very quickly to find a propagation on the spectrum of HF and VHF bands.

The chart of the receiver is shown on **Figure 1**. Receiver includes balanced mixer (1), low-pass filter (2), high-pass filter (3), VFO that works at 16- 33 MHz (4), superregenerative detector aka IF amplifier on 45 MHz (6). Switched filters are formed a working band of the receiver (HF or VHF). The receiver has two struck points. First lays on 22. 5 MHz the second one is on 65.5 MHz. If you want to have reception on the frequencies just move the IF of the receiver (with help of C11) up or down.

**Figure 1.** Chart of the simple SWL receiver

**Note:** The figure is original scan from the “DX Reception” book. English commentary are given inside oval.

The simplicity of design of the receiver and its high sensitivity (just at connection of an antenna in 1 meter length the receiver provides satisfactory reception on the HF and VHF bands) is reached by a superregenerative detector. However the superregenerative detector gives basic lacks of the receiver – low selectivity and low dynamic range. There is no SSB reception. **Figure 2** shows the circuit diagram for low-pass (**Fig. 2a**) and high-pass (**Fig. 2b**) filters. The filters were made for 50 (75) input/ 50 (75) Ohms output, i.e., the filters require a 50 (75) Ohms antenna and mixer having 50 (75) Ohms input. SBL-1 is okay for that. However the receiver works well with an antenna having almost any input impedance. **Figure 3** shows the circuit diagram for the receiver. If you have no SBL- 1 you may do the mixer according to **Figure 3**.

**Figure 2.** Circuit diagram for low-pass (**Fig. 2a**) and high-pass (**Fig. 2b**) filters  
(Values for all capacitors are given in picofarads)

**Note:** The figure is original scan from the “DX Reception” book. English commentary are given inside oval.

**Figure 3.** Circuit diagram for simple SWL receiver

**Note:** The figure is original scan from the “DX Reception” book. English commentary are given inside oval.

**Table 1** shows data for inductors of the receiver and filters. All coils are wound by insulated copper wire in diameter 1-mm (18 -AWG), all coils are air-wound. The filters are assembled in a box (80X40X40- mm) soldered from two- sided PCB. The receiver is assembled in a box (155x 90x 55- mm), soldered from two- sided PCB. **Figure 4** shows component layout for the receiver. The components are sitting on the wiring strips from an old tube receiver. When the receiver will be tuned close the box, where the receiver is assembled, by a plate of a PCB. The plate should be soldered at several places to the box.

**Figure 4** Components layout for simple SWL receiver

### Design and Tuning

**Low-pass and high-pass** filter made strictly to **Table 1** and **Figure 4** does not require any tuning.

**VFO** made from good parts according to the schematic works straight away. Only the tuning is the set up of the frequencies range. Needed frequencies range do rough by the pressing- stretching of the L9, fine with the C2. Arrange L10 near L9 to maxima and equal across the band sensitivity.



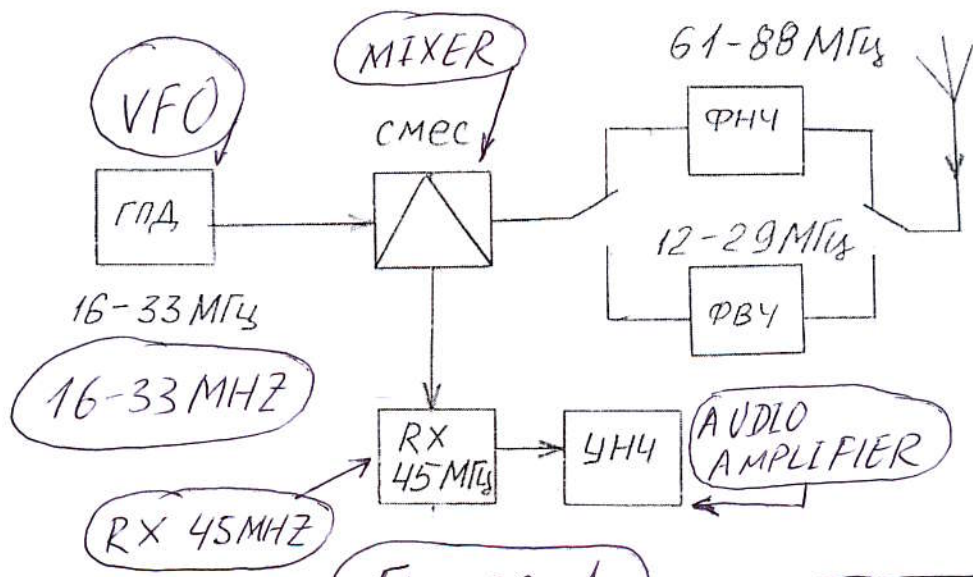


Figure 1

English \*  
commentary

РЧЧ 1


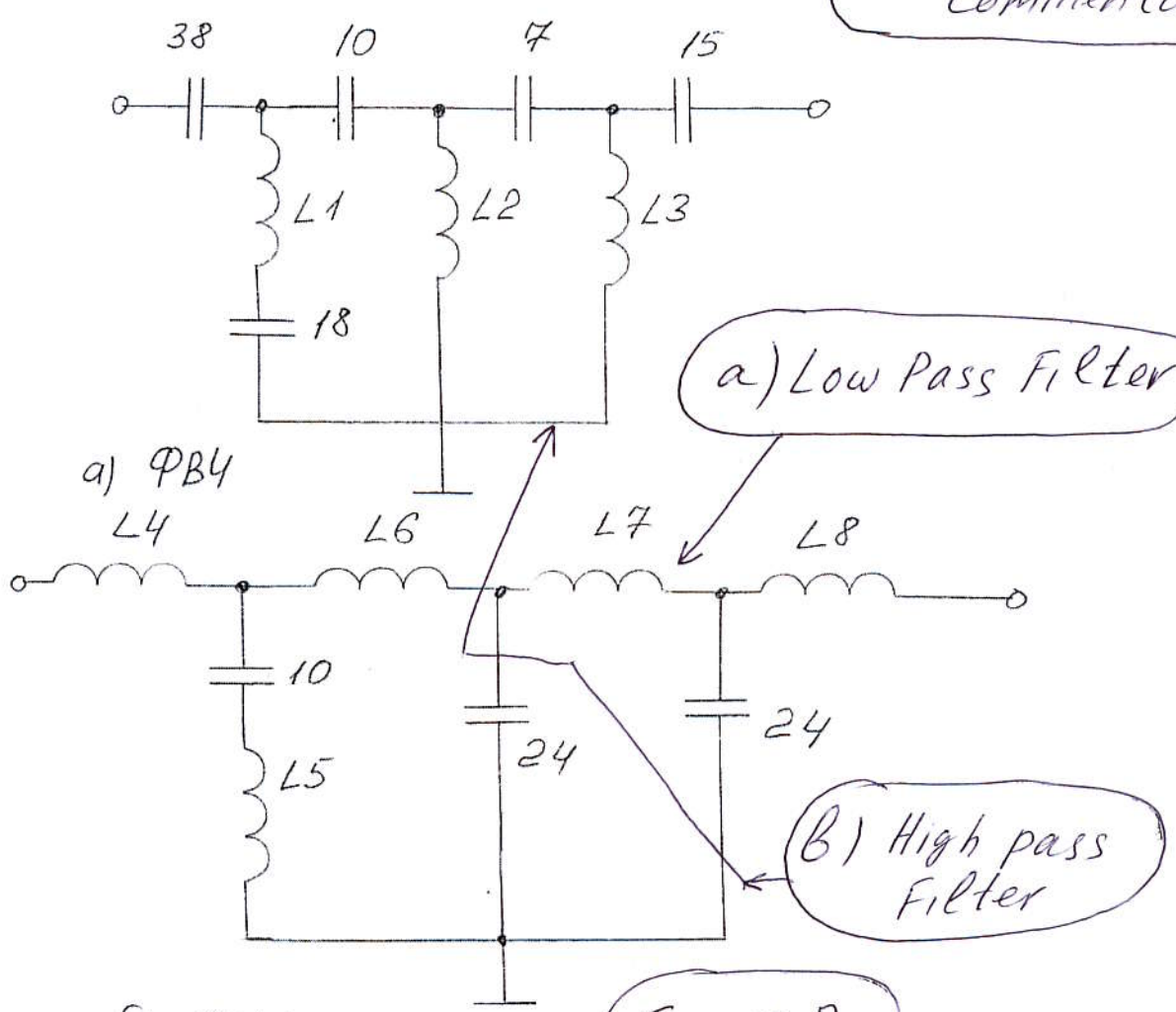


Figure 2

б) ФНЧ  
РЧЧ 2

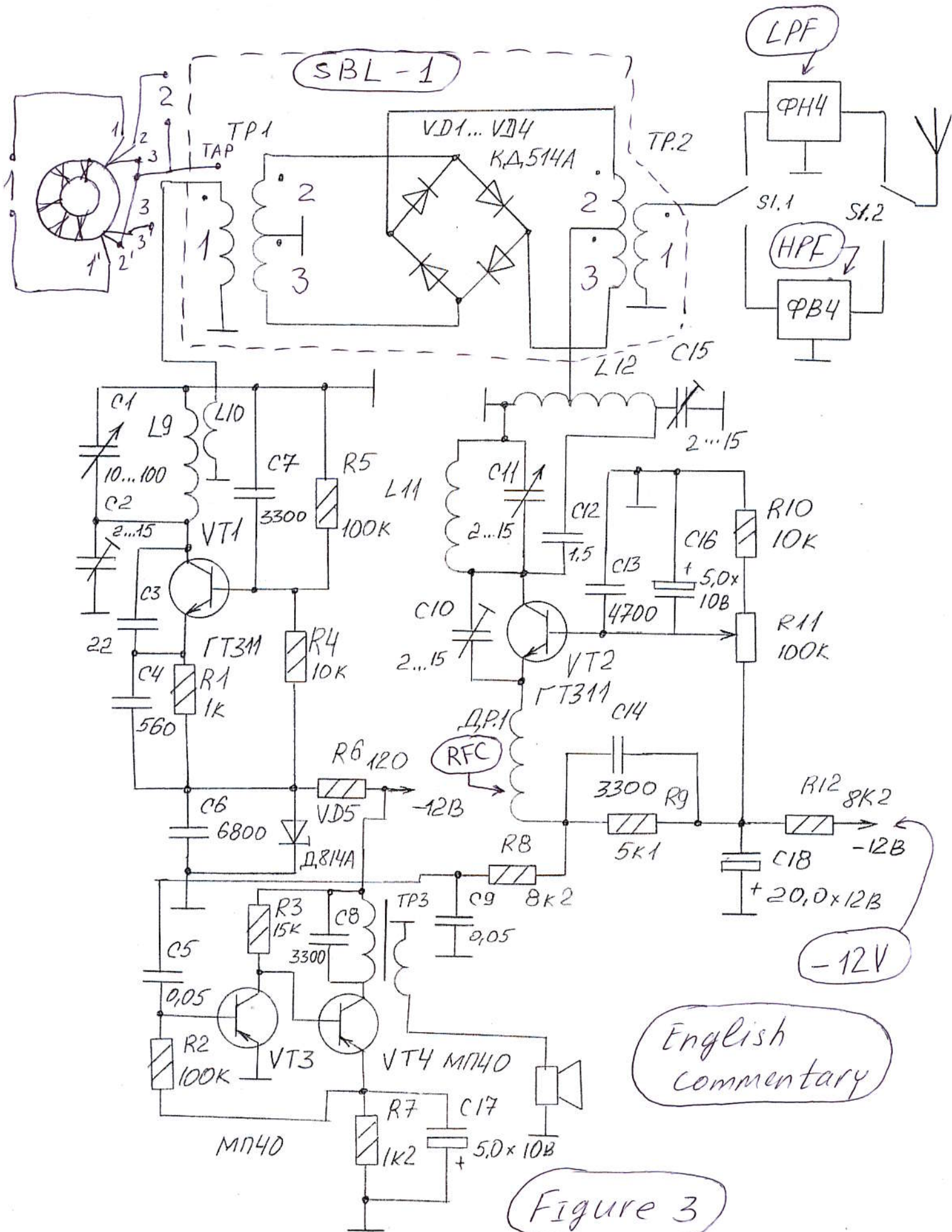

English commentary

Figure 3

English  
commentary\*

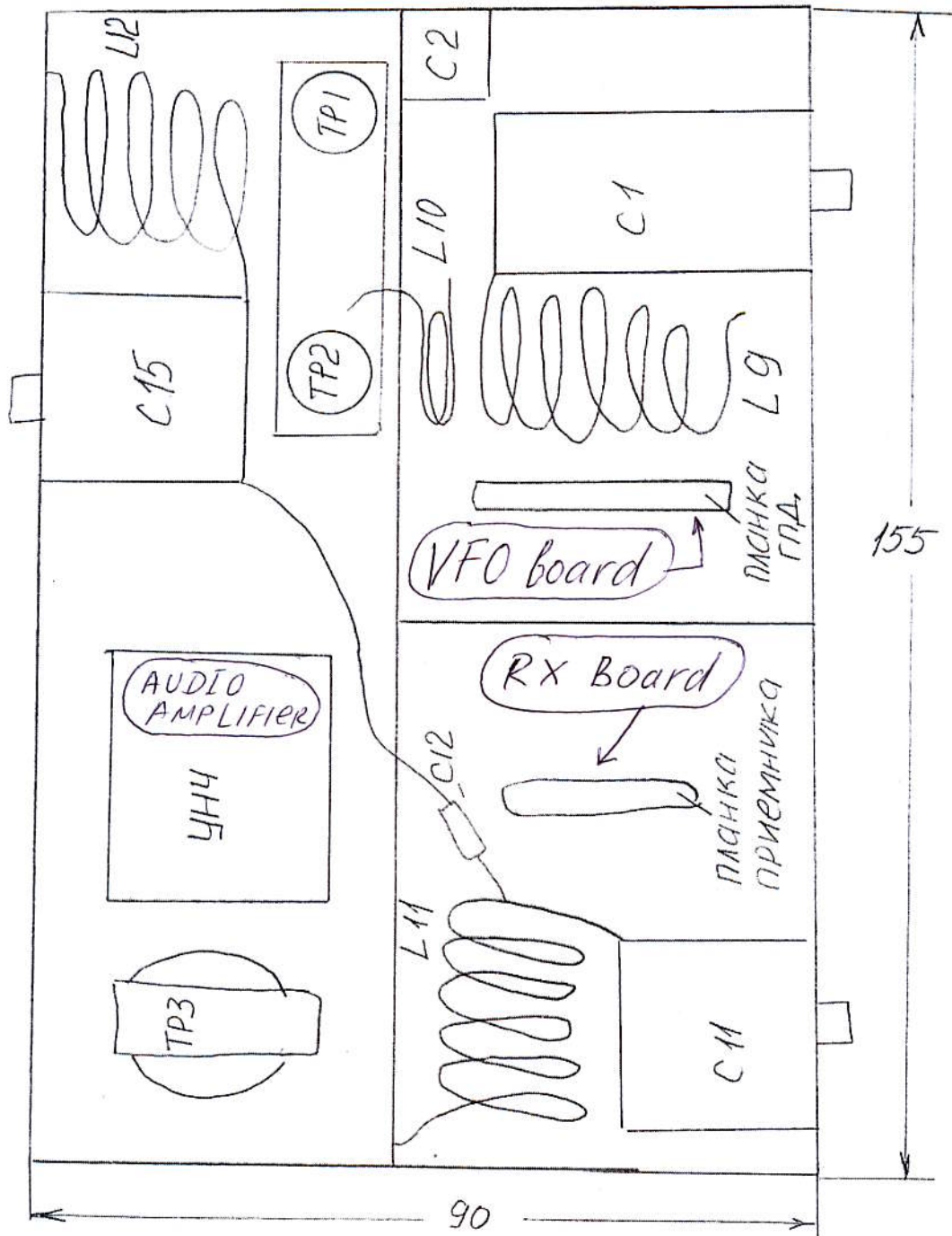


РИС. 4

Figure 4

Table 1. Data for inductors

# Inductor	Diameter of the Inductor, mm	Length of winding, mm	Quantity of Coils	Note
L1	14	10	8	Athwart to L2, L3
L2, L3	14	20	7	
L4	14	5	4	
L5	14	10	7	Athwart to L6, L7, L8
L6	14	20	11	
L7	14	20	14	
L8	14	10	6	
L9	18	25	7.5	
L10	18	4	2	Near "cold" end L9
L11, L12	18	14	8	Tap from 2 Turn from "cold" end

**Superregenerative stage** adjusted with R11 and C10. When superregenerative stage is working properly you hear specific noise in the speaker. Frequency of the stage (IF) set up with help of C11. After that do tuning L12C15 to maxima sensitivity of the receiver.

**Audio Amplifier** made from good parts according to the schematic works straight away. Almost any low power, low noise (better high- gain) transistors work well at the receiver. Transformer TP3 was used from an old transistor radio. Was used a 16 Ohms Speaker from an old transistor radio. It is possible (ever better) switch on a high- impedance head phone instead the TP3.

### Parts List

#### Resistors:

R1: 1 k  
 R2: 100 k  
 R3: 15 k  
 R4: 10 k  
 R5: 100 k  
 R6: 120 Ohm  
 R7: 1.2 k  
 R8: 8.2 k  
 R9: 5.1 k  
 R10: 10 k  
 R11: 100 k , potentiometer  
 R12: 8.2 k

R10: 10 k  
 R11: 100 k , potentiometer  
 R12: 8.2 k

K = multiply to 1000 Ohm  
 All resistors 0.125 W

#### Capacitors:

C1: Variable, air dielectric, 10- 100 pF  
 C2: Variable, air dielectric, 2- 15 pF  
 C3: 22 pF  
 C4: 560 pF  
 C5: 0.05 uF  
 C6: 6800 pF  
 C7: 3300 pF  
 C8: 3300 pF

## ANTENTOP- 01- 2007, # 009

C9: 0.05  $\mu$ F  
C10: Variable, air dielectric, 2- 15 pF  
C11: Variable, air dielectric, 2- 15 pF  
C12: 1.5 pF  
C13: 4700 pF  
C14: 3300 pF  
C15: Variable, air dielectric, 2- 15 pF  
C16: 5.0  $\mu$ F/ 10V  
C17: 5.0  $\mu$ F/ 10V  
C18: 20.0  $\mu$ F/ 12V

Polarized capacitors are electrolytic

### Diodes:

VD1... VD4: Any small low power RF Schottky diodes  
VD5: Zener diode 9.0V/15 mA

### Transformers:

TP1, TP2: Core: Amidon analog is T37- 10  
10 turns by trifilar insulated wire OD 0.15 mm (34 AWG),  
winding to 1 cm length.  
Uniformly onto the core.  
So, primary winding 1- 10 turns, secondary winding 2- 10  
third winding 3- 10 turns.  
● – winding phase

## Simple SWL HF- VHF Receiver

TP3: Audio transformer from an old transistor radio  
**Note:** Diodes VD1- VD4 and transformers TP1 and  
TP2 may be changed to IC SBL-1.

### Transistors:

VT1: Small power RF germanium transistor, gain 80-  
100, upper frequency 250 MHz  
May be changed to silicon transistor with equal data.  
VT2: Small power RF germanium transistor, gain 80-  
100, upper frequency 250 MHz  
May be changed to silicon transistor with equal data.  
VT3, VT4: Any high gain (100- 200) small power  
transistors

### Switch:

S1: Any Toggle DPDT

### RF Choke

RFC: OD: 3.5... 5 (not critical)mm  
Length of winding: 15... 20 (not critical)mm  
Coiled by insulated wire OD 0.15 mm (34 AWG)  
Winding: Turn to turn, uniformly

**73! I.G.**



**From forum QRP- ARCI  
(QRP- F- Forum)**

**Posted by:** [John AE5X](#),

**Posted On:** 07/15/07,

**Subject:** Russian  
woodpecker antenna

From UA0AAM here is the  
antenna used at one of the  
radar sites that we copy on  
the ham bands at times. I'd  
sure love to have this baby  
on 40m some winter evening.  
I wonder if it's rotatable...?