

PA 3xGU50. Photos of the Design


N. Kisel, UA3AIC,
Moscow, Russia
ua3aic@mail.ru

Credit Line: www.cqham.ru

Photos step by step show how to do simple PA 3xGU50.

Schematic of the PA is shown on **Figure 1**.

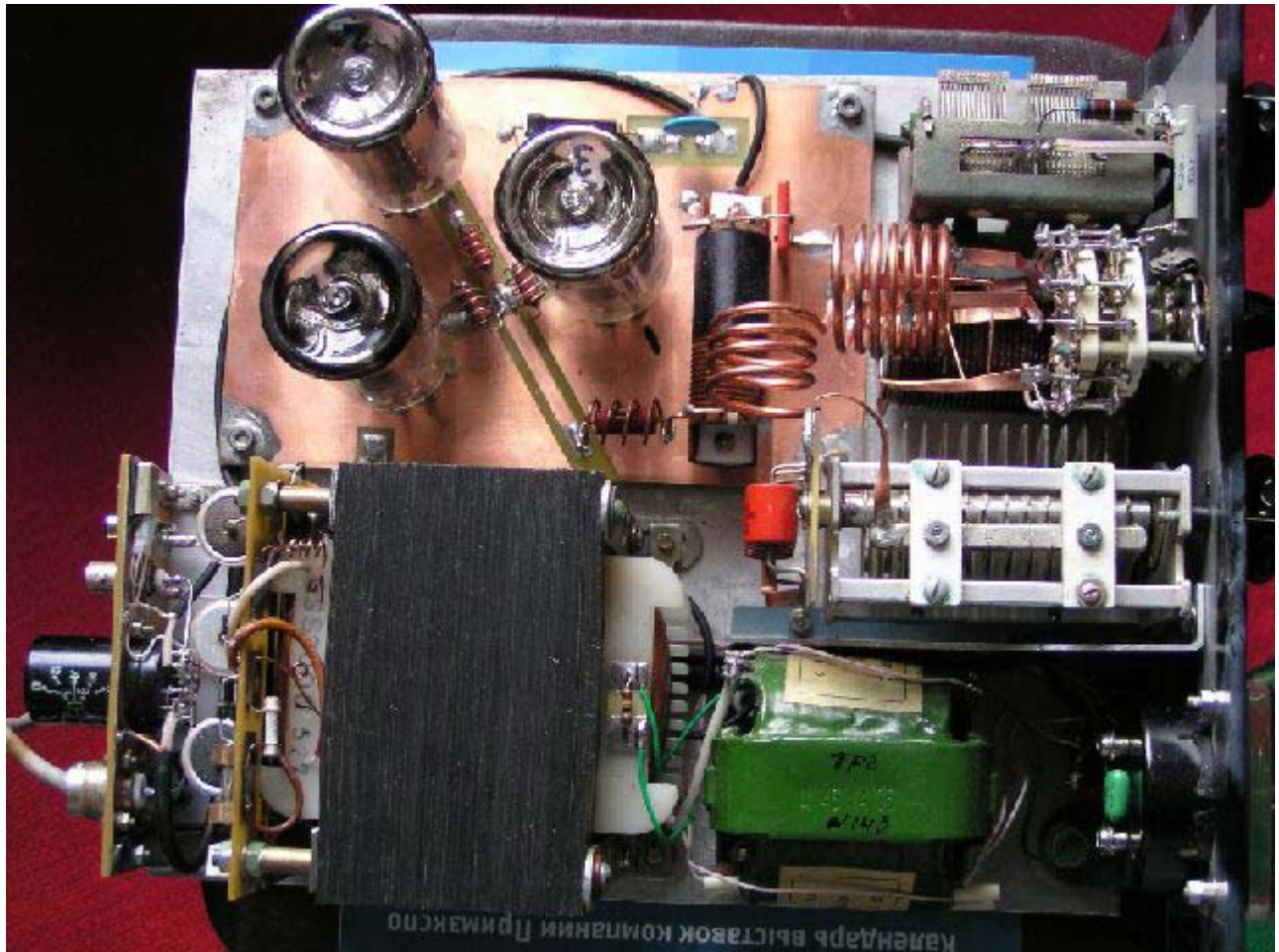Copper foil for tap used from a power coaxial cable. If for the PA two sided PC-board is used you should remove foil from back side opposite to anode trace. The path free from foil should be in 15-20 mm wide.



www.cqham.ru

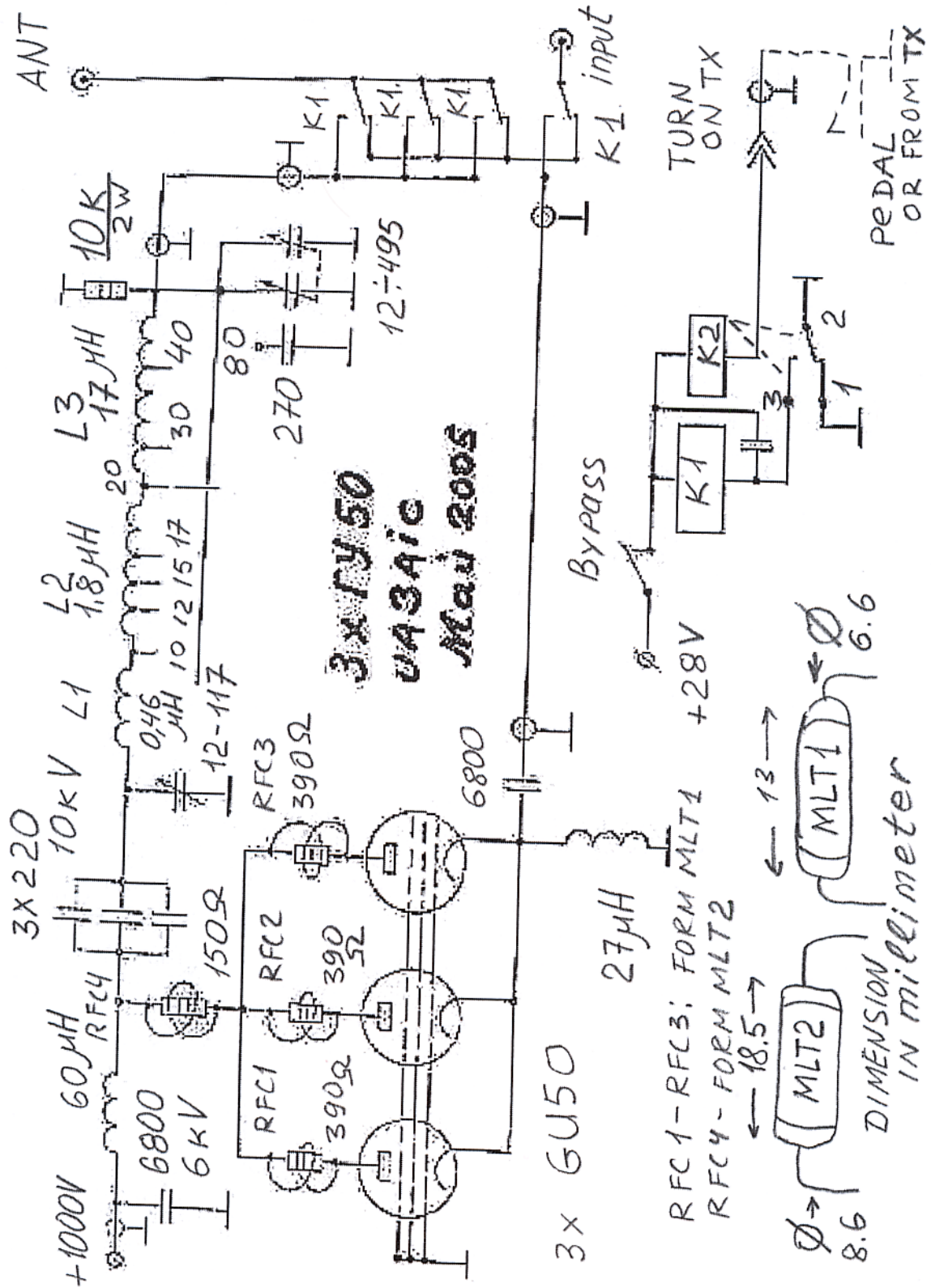


Figure 1 PA 3xGU50

ANTENTOP

FREE e- magazine edited by hams for hams
 Devoted to Antennas and Amateur Radio
www.antentop.org

