

# Antenna Tuner for Symmetrical Two Wire Line


By: *Andrey Radchenko, UR3ILF*

Very interesting practical design of the *Antenna Tuner for Symmetrical Two Wire Line* it was published in the Forum at CQHAM.RU.

Andrey wrote: I made antenna tuner on schematic shown on **Figure 1** just for one evening. The schematic was introduced by *PA0FRI*, it is TravelS Match.

However, instead of the T200- 2 I used T157- 2. Those ferrite rings are easy to obtain and cheaper then T200-2 but less in diameter that may reduce the power what the ATU may stand. The *Photo* shows design of the tuner. Tuner works well on all HF-Bands.

*73! de UR3ILF*

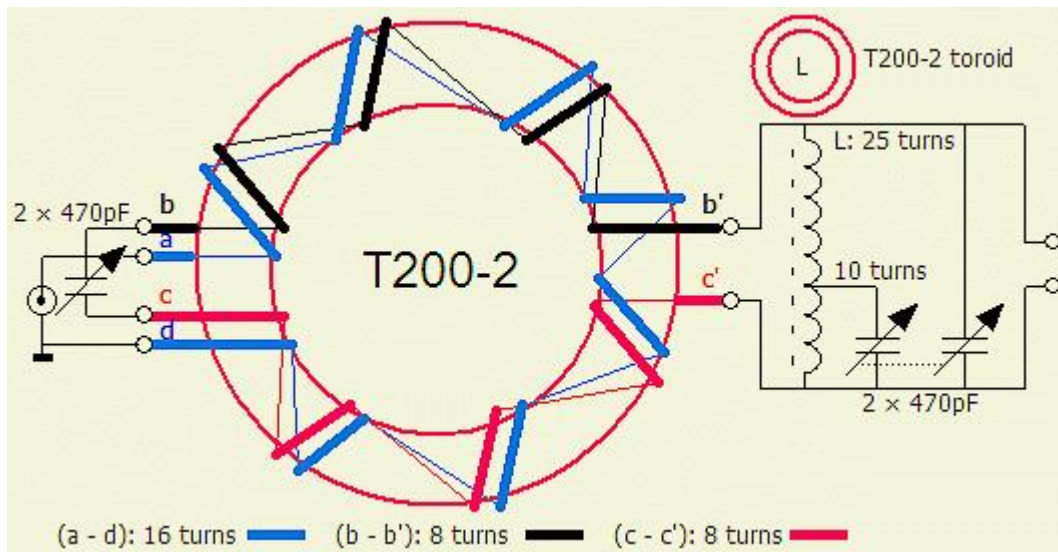

**Figure 1** Travel S- match by PA0FRI

